
Computer Architecture & Assembly Language 14:332:331

Lecture 6 The Processor

Naghmeh Karimi
Fall 16


Adapted from *Computer Organization and Design, 5th Edition*, Patterson & Hennessy, © 2013, Elsevier, and *Computer Organization and Design, 4th Edition*, Patterson & Hennessy, © 2008, Elsevier and Mary Jane Irwin's slides from Penn State University.

Introduction

- CPU performance factors
 - Instruction count
 - Determined by ISA and compiler
 - CPI and Cycle time
 - Determined by CPU hardware
- We will examine two MIPS implementations
 - A simplified version
 - A more realistic pipelined version
- Simple subset, shows most aspects
 - Memory reference: l w, s w
 - Arithmetic/logical: add, sub, and, or, sl t
 - Control transfer: beq, j

The Processor: Datapath & Control

 - Generic implementation:
 - use the program counter (PC) to supply the instruction address and fetch the instruction from memory (and update the PC)
 - decode the instruction (and read registers)
 - execute the instruction
- All instructions (except `j`) use the ALU after reading the registers




Instruction Execution

- PC \rightarrow instruction memory, fetch instruction
- Register numbers \rightarrow register file, read registers
- Depending on instruction class
 - Use ALU to calculate
 - Arithmetic result
 - Memory address for load/store
 - Branch target address
 - Access data memory for load/store
 - PC \leftarrow target address or PC + 4

Abstract Implementation View

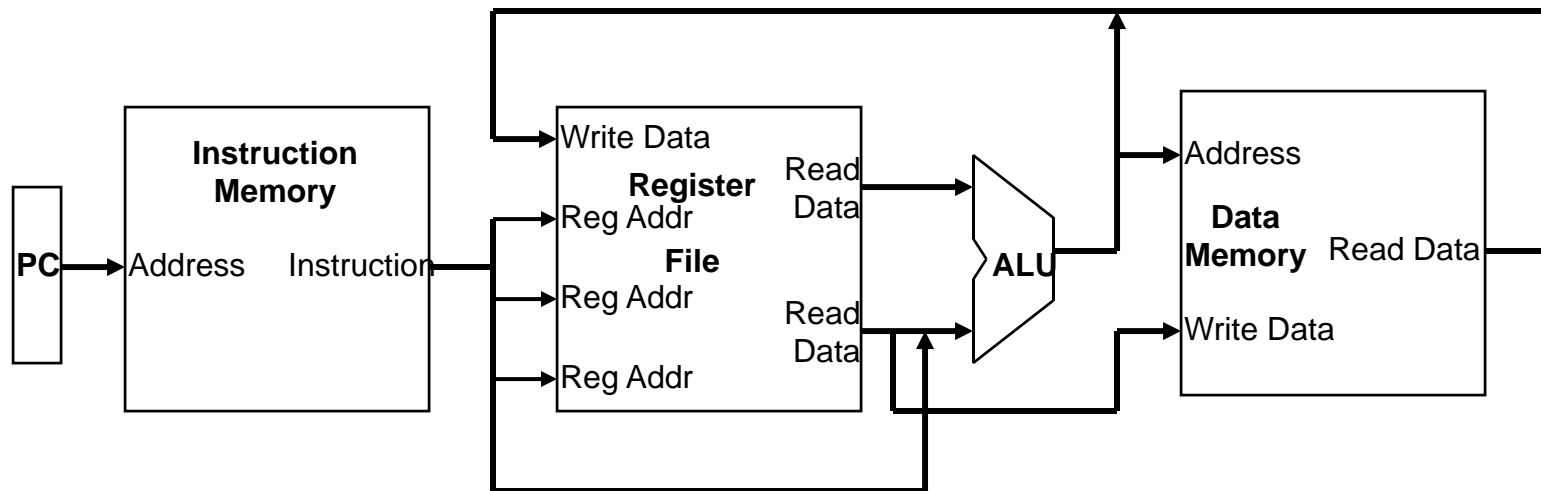
- Two types of functional units:
 - elements that operate on data values (combinational)
 - elements that contain state (sequential)



- Single cycle operation
- Split memory (Harvard) model - one memory for instructions and one for data

Clocking Methodologies

 - Clocking methodology defines when signals can be read and when they can be written



clock rate = $1/(\text{cycle time})$

e.g., 10 nsec cycle time = 100 MHz clock rate


1 nsec cycle time = 1 GHz clock rate

□ State element design choices

- level sensitive latch
- master-slave and edge-triggered flipflops



Review: State Elements

- Set-reset latch

 

S	R	$Q(t+1)$	$!Q(t+1)$
0	1	0	1
1	0	1	0
0	0	$Q(t)$	$!Q(t)$
1	1	0	0


- Level sensitive D latch

  

- latch is transparent when clock is high (copies input to output)

Review: State Elements, con't

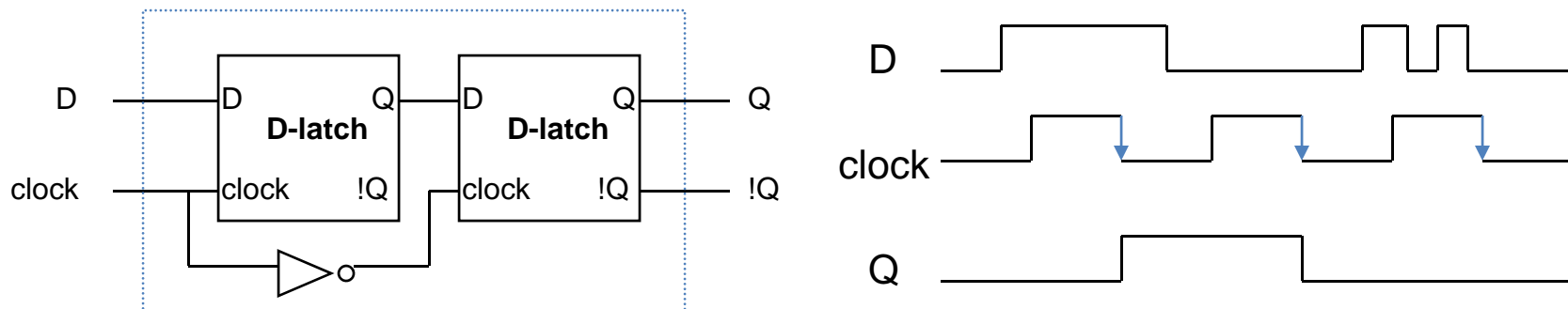
- Solution is to use flipflops that change state (Q) only on clock edge (master-slave)



- Master (first D-latch) copies the input when the clock is high (the slave (second D-latch) is locked in its memory state and the output does not change)
- Slave copies the master when the clock goes low (the master is now locked in its memory state so changes at the input are not loaded into the master D-latch)
- Must have the clock cycle time long enough to accommodate the worst case delay path


Our Implementation

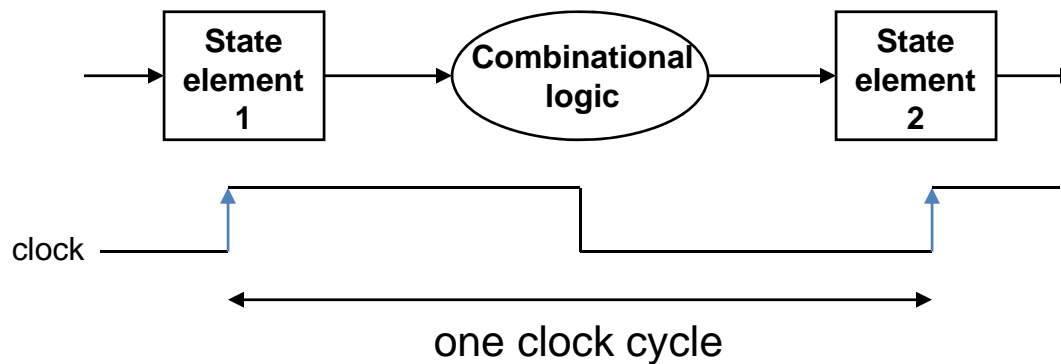- An edge-triggered methodology
- Typical execution
 - read contents of some state elements
 - send values through some combinational logic
 - write results to one or more state elements




- Assumes state elements are written on every clock cycle; if not, need explicit write control signal
 - write occurs only when both the write control is asserted and the clock edge occurs

Instruction Fetch

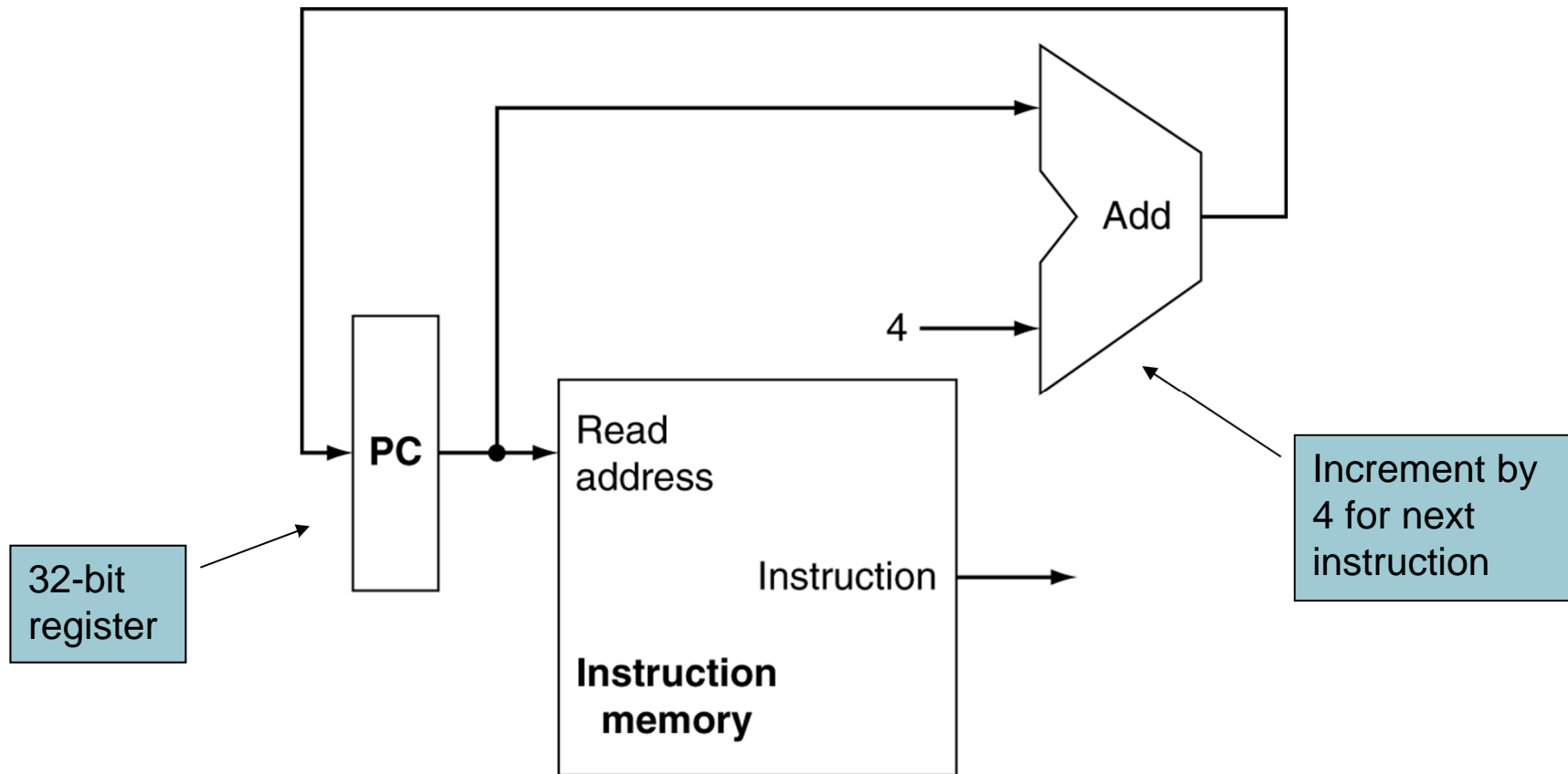

Fetching Instructions

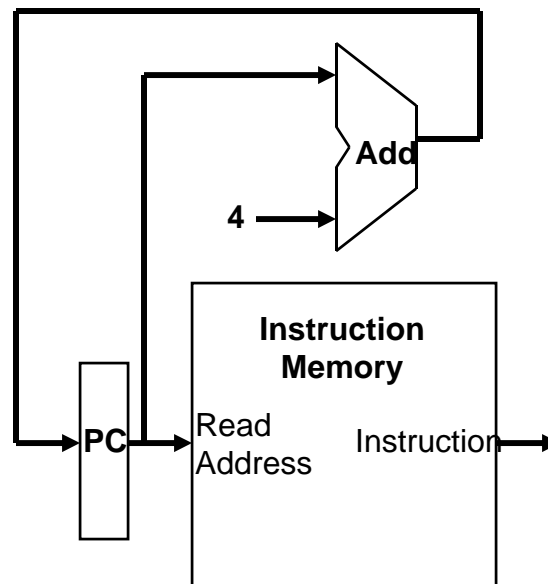
- Fetching instructions involves
 - reading the instruction from the Instruction Memory
 - updating the PC to hold the address of the next instruction



- PC is updated every cycle, so it does not need an explicit write control signal
- Instruction Memory is read every cycle, so it doesn't need an explicit read control signal

Decoding Instructions

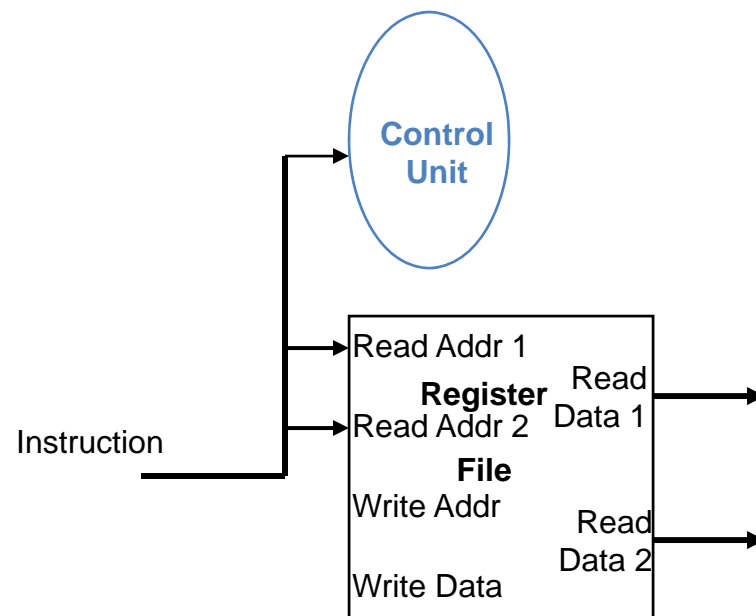
- Decoding instructions involves
 - sending the fetched instruction's opcode and function field bits to the control unit




- **reading two values from the Register File**
 - **Register File addresses are contained in the instruction**

R-Format Instructions

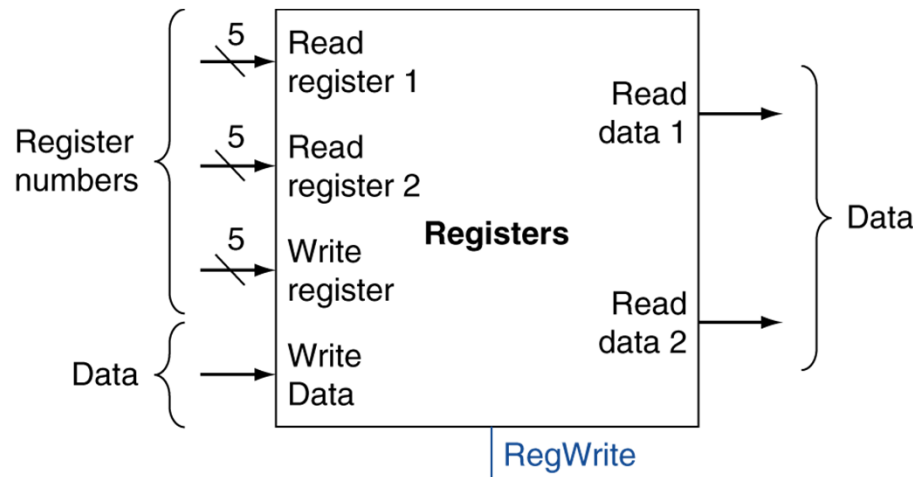- Read two register operands
- Perform arithmetic/logical operation
(indicated by op and funct)
- Write register result




a. Registers

 

 
b. ALU

Executing R Format Operations

- R format operations (`add`, `sub`, `slt`, `and`, `or`)



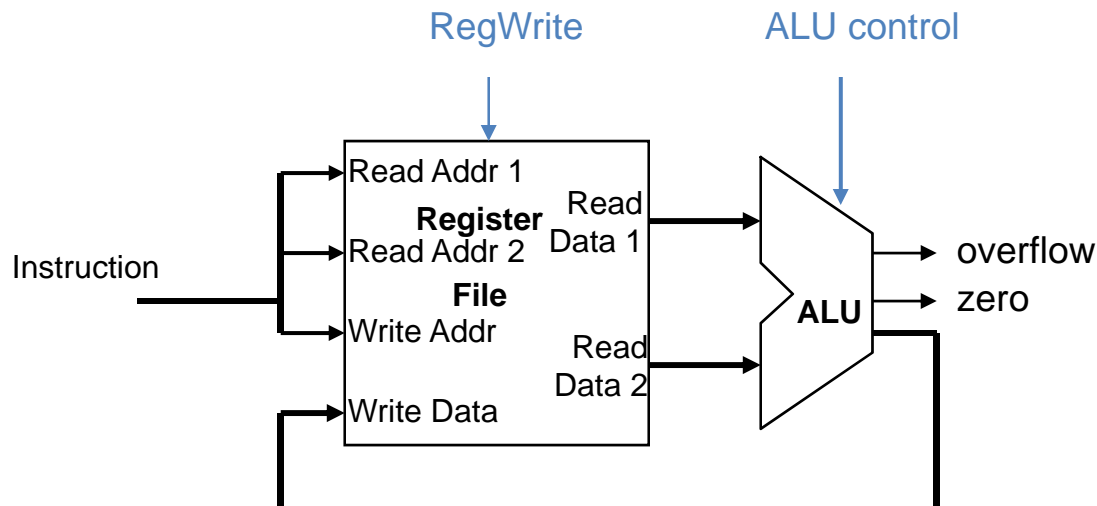
- perform the indicated (by `op` and `funct`) operation on values in `rs` and `rt`
- store the result back into the Register File (into location `rd`)



- Note that Register File is not written every cycle (e.g. `sw`), so we need an explicit write control signal for the Register File

Executing Load/Store Operations


- Load and store operations

 


- compute a memory address by adding the base register (in rs) to the 16-bit signed offset field in the instruction
 - base register was read from the Register File during decode
 - offset value in the low order 16 bits of the instruction must be sign extended to create a 32-bit signed value
- **store value**, read from the Register File during decode, must be written to the Data Memory
- **load value**, read from the Data Memory, must be stored in the Register File

Load/Store Instructions

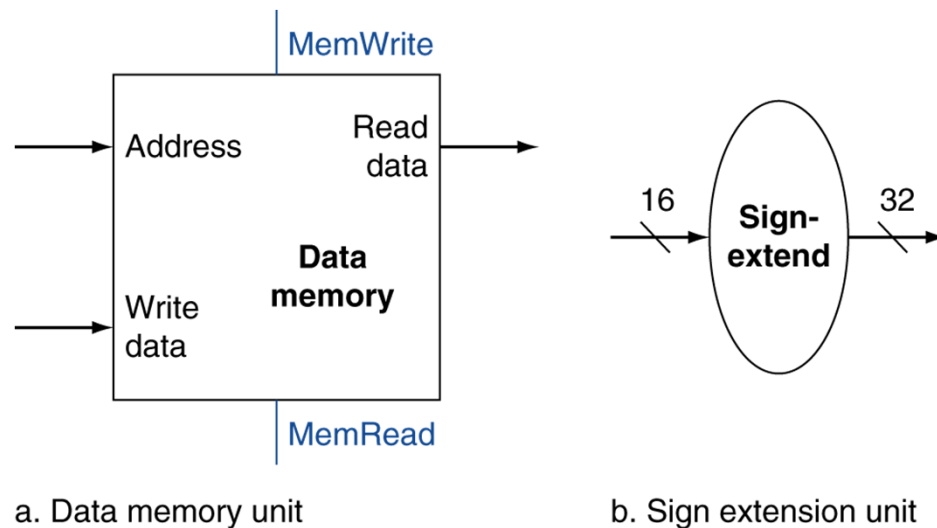- Read register operands
- Calculate address using 16-bit offset
 - Use ALU, but sign-extend offset
- Load: Read memory and update register
- Store: Write register value to memory




Executing Load/Store Operations, con'd

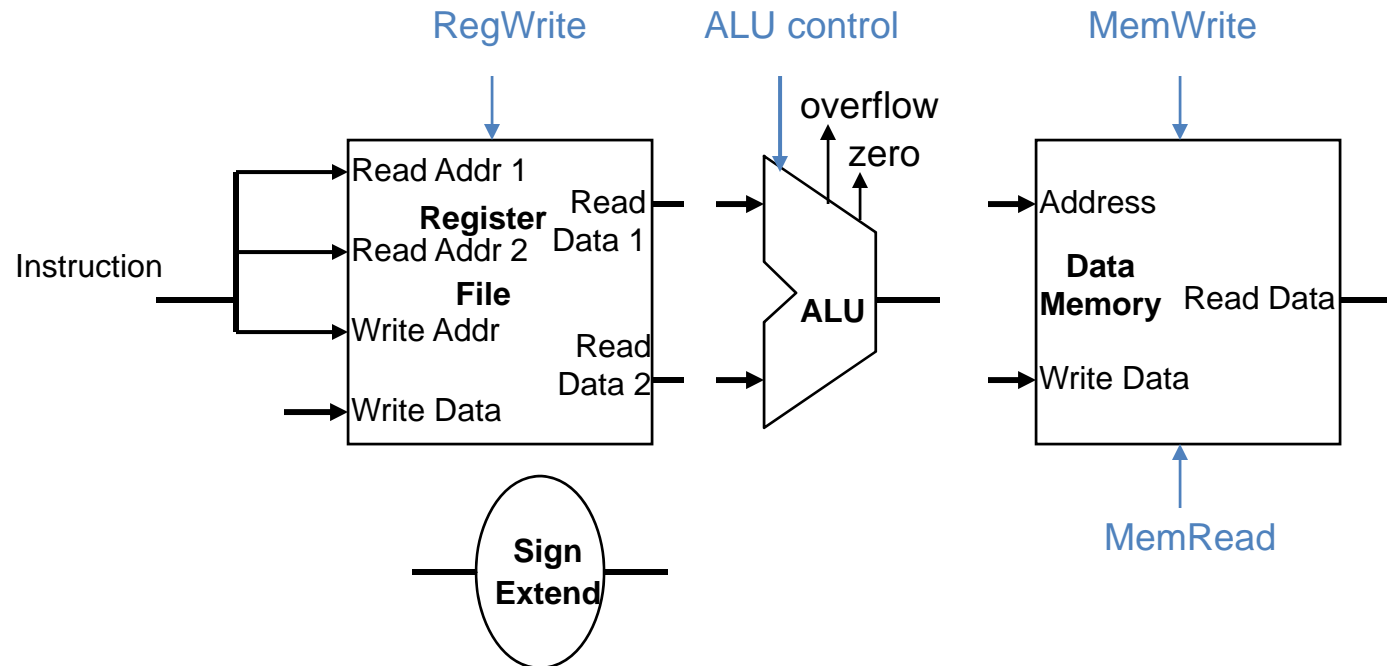


Executing Branch Operations

- Branch operations have to

 


- compare the operands read from the Register File during decode (rs and rt values) for equality (**zero** ALU output)
- compute the branch target address by adding the updated PC to the sign extended 16-bit signed offset field in the instruction
 - “base register” is the **updated** PC
 - offset value in the low order 16 bits of the instruction must be sign extended to create a 32-bit signed value and then shifted left 2 bits to turn it into a word address

Branch Instructions

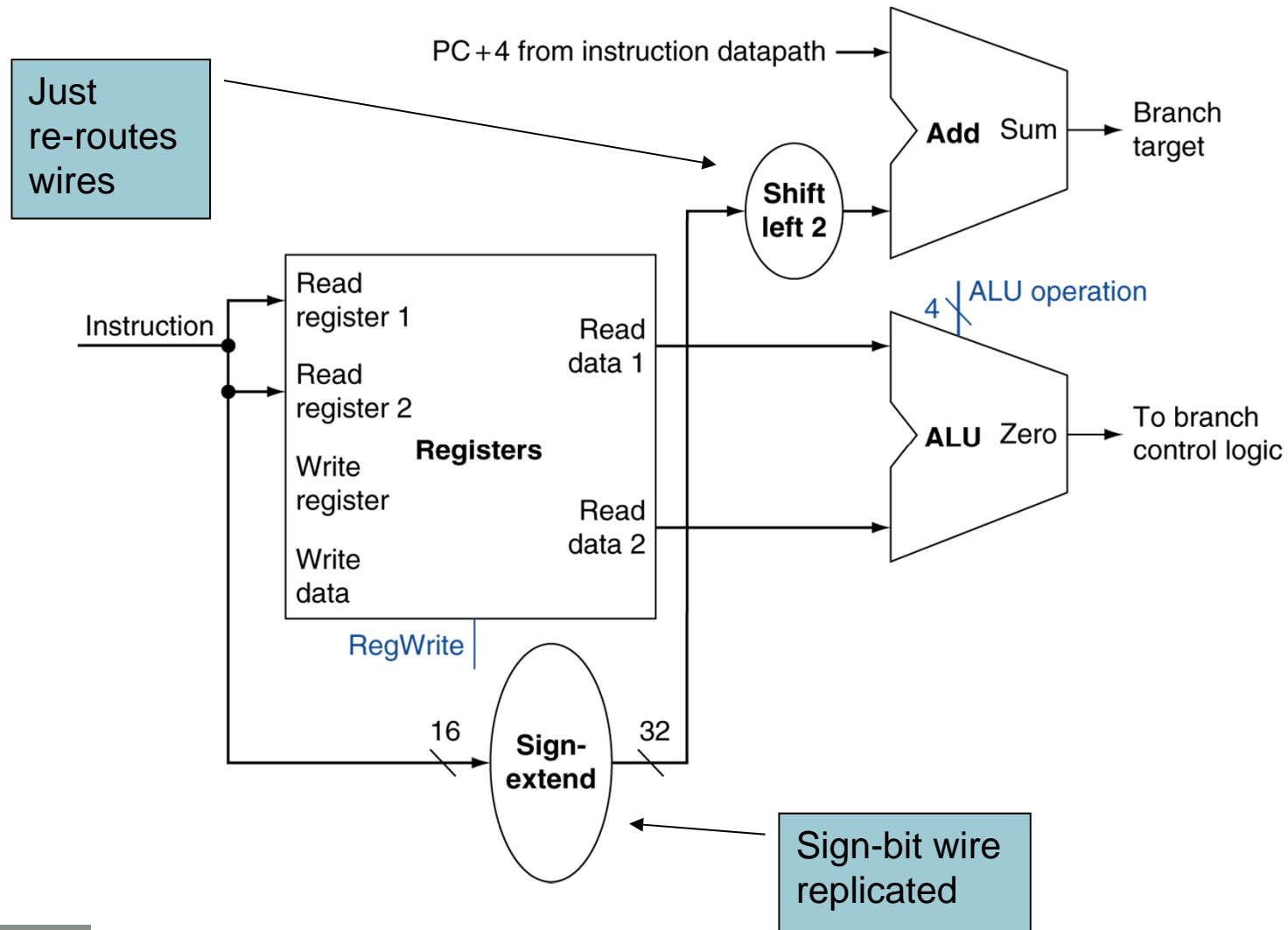


Implementing Jumps

 

- Jump uses word address
- Update PC with concatenation of
 - Top 4 bits of old PC
 - 26-bit jump address
 - 00
- Need an extra control signal decoded from opcode

Executing Jump Operations

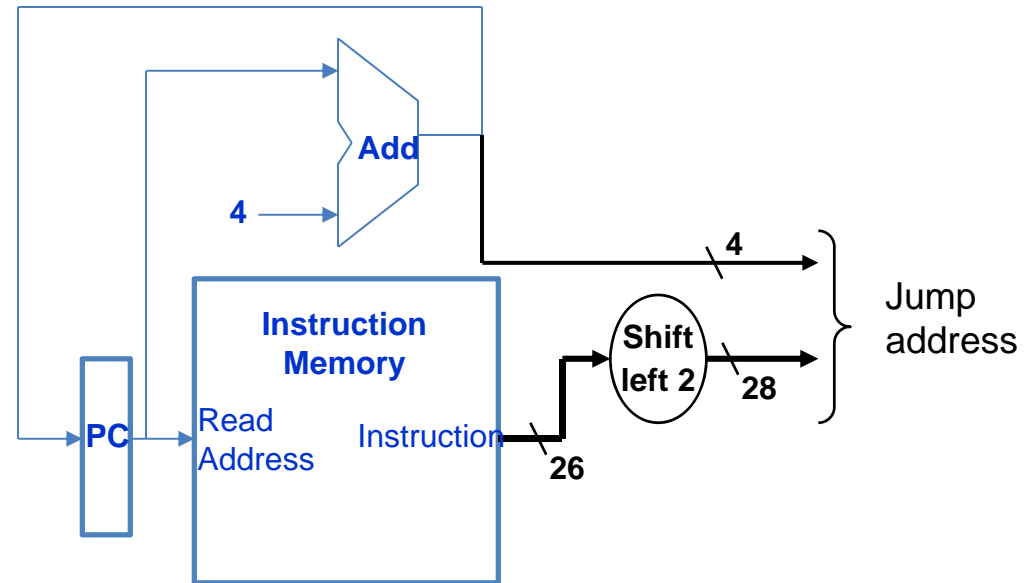


Our Simple Control Structure


- We wait for everything to settle down
 - ALU might not produce “right answer” right away
 - we use write signals along with the clock edge to determine when to write (to the Register File and the Data Memory)
- Cycle time determined by length of the longest path

We are ignoring some details like register setup and hold times


Fetch, R, and Memory Access Portions

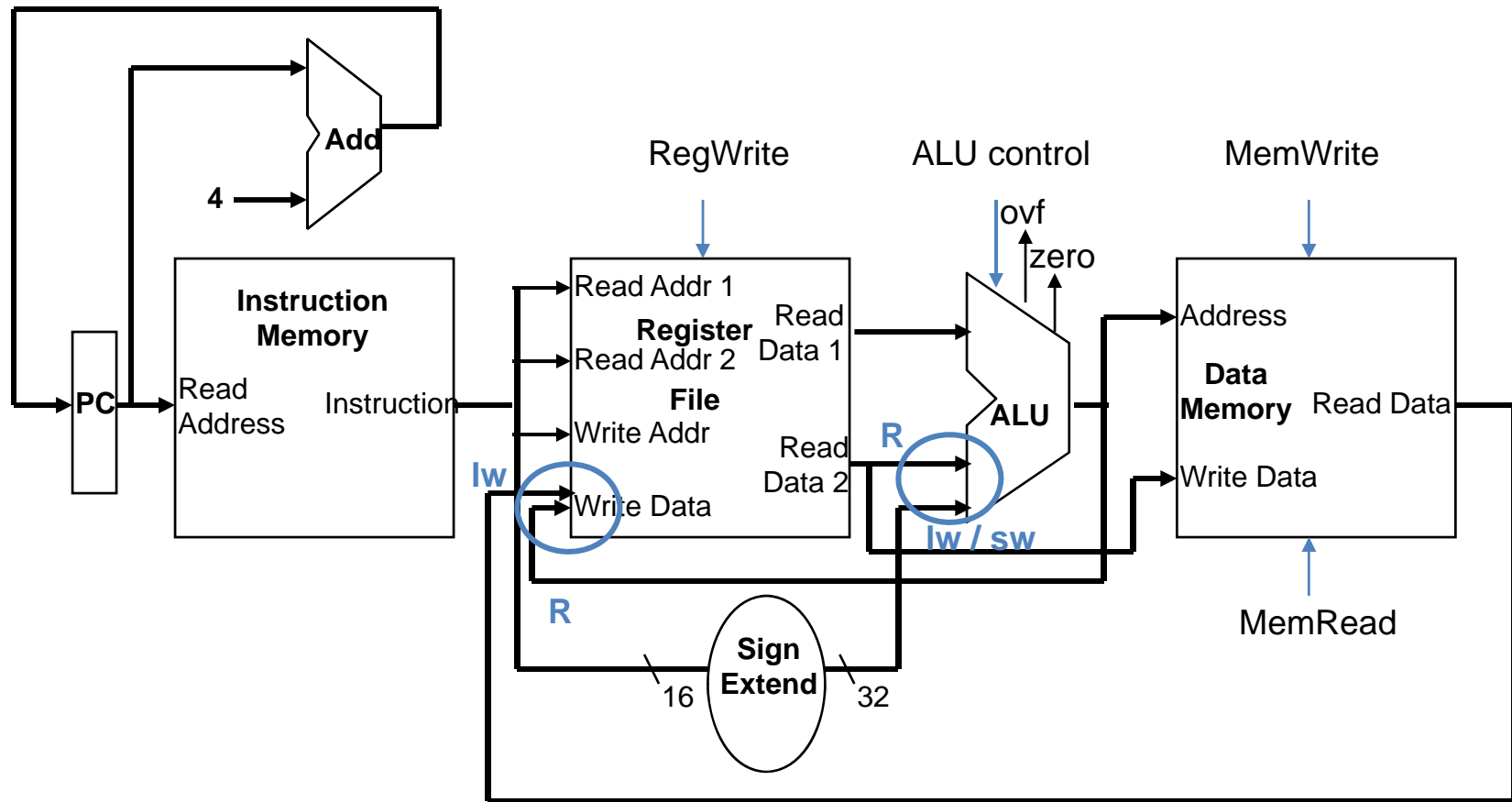


Multiplexor Insertion

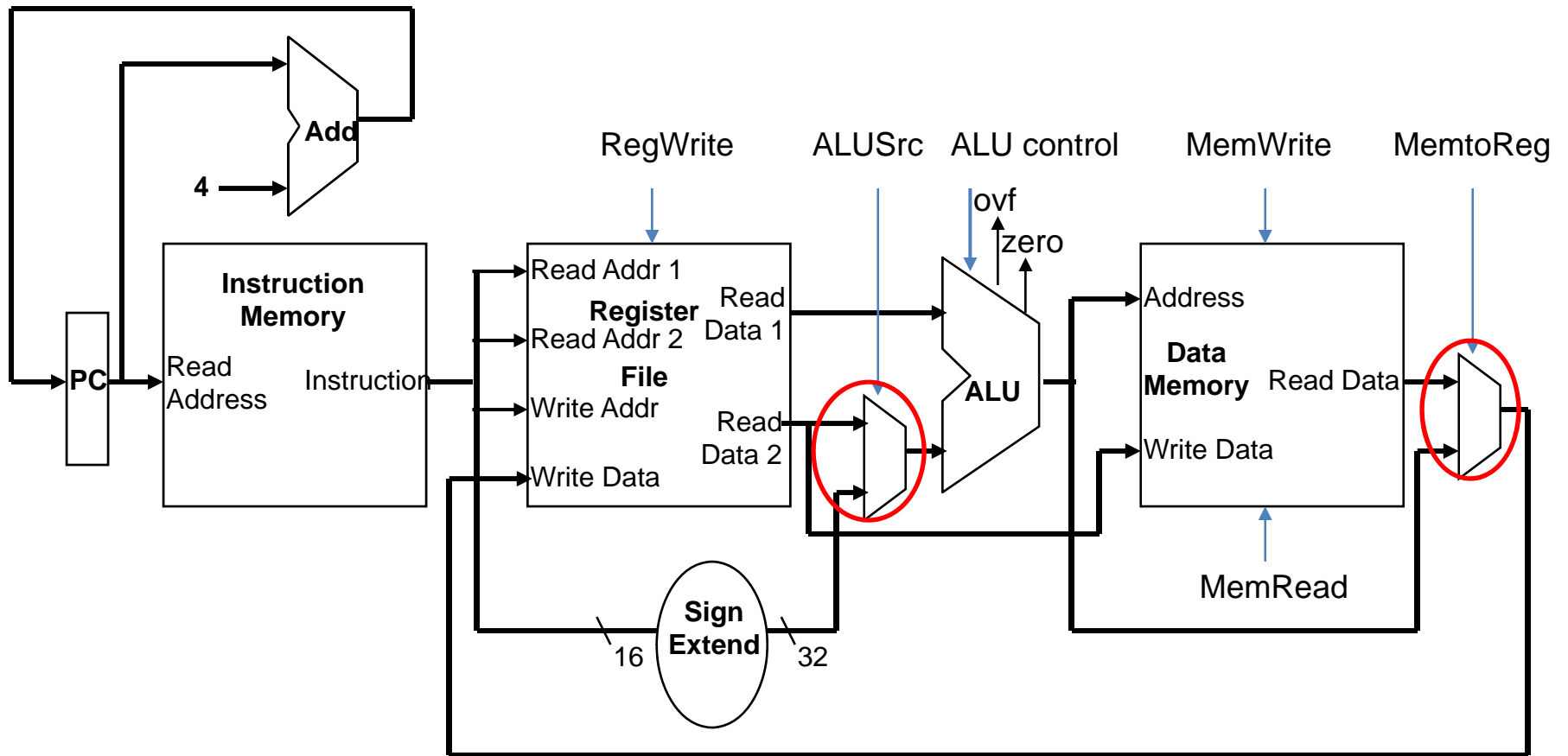

Adding the Branch Portion

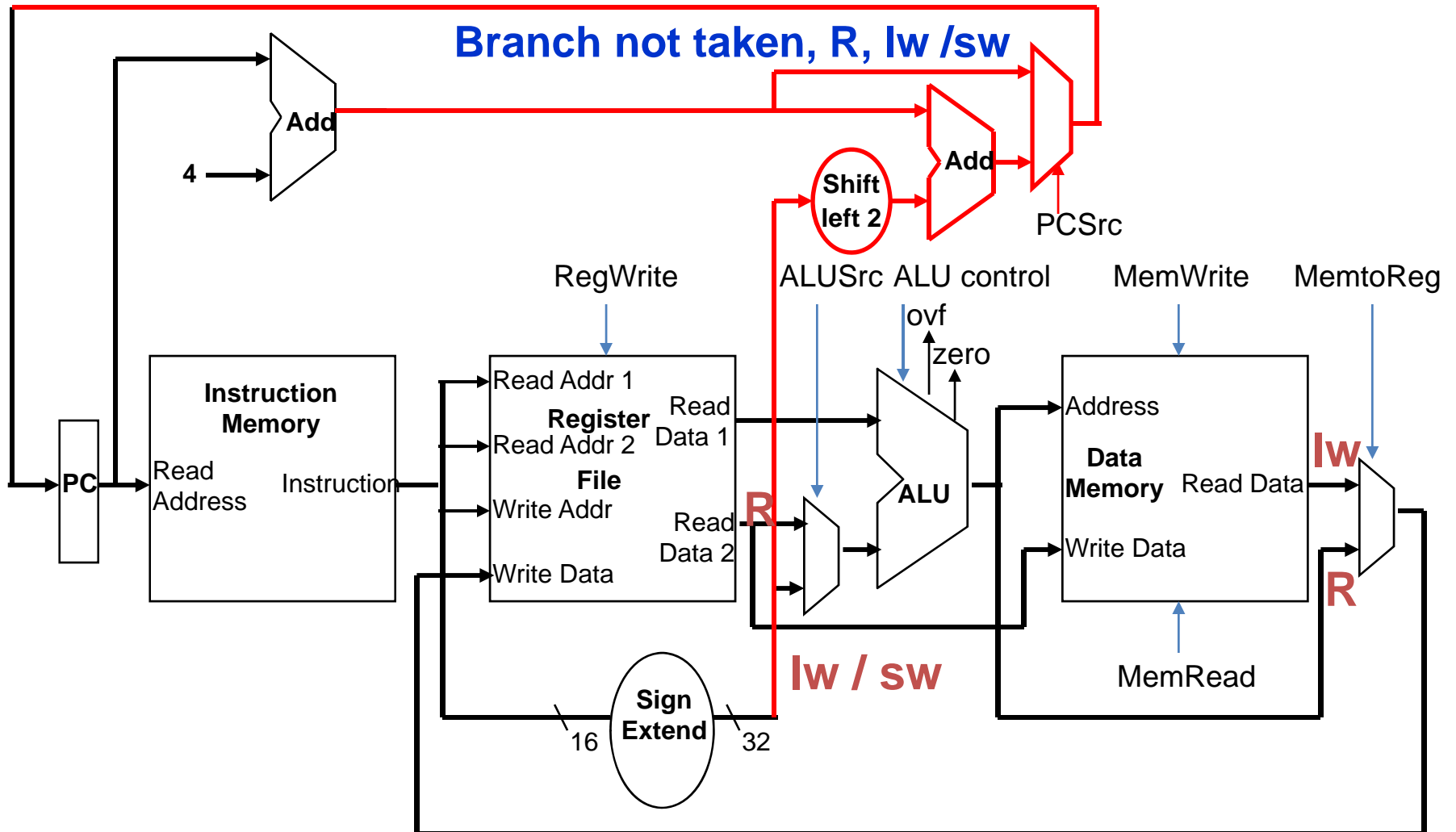

Full Datapath

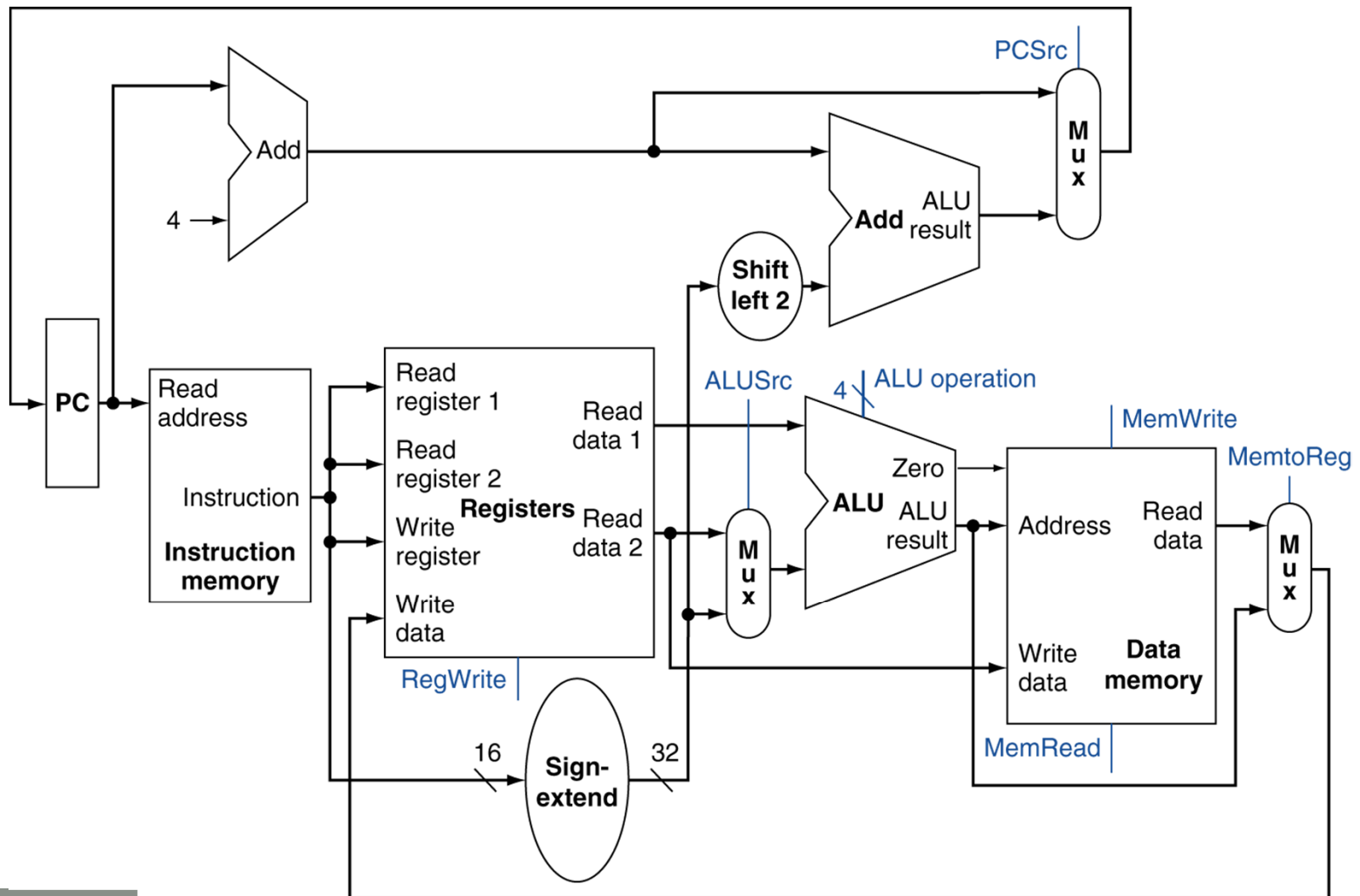

Review



- ❑ **Split memory (Harvard) model - single cycle operation**
- ❑ **Simplified to contain only the instructions:**
 - memory-reference instructions: `lw, sw`
 - arithmetic-logical instructions: `add, sub, and, or, slt`
 - control flow instructions: `beq, j`
- ❑ **Sequential components (PC, RegFile, Memory) are edge triggered**
 - state elements are written on every clock cycle; if not, need explicit write control signal
 - write occurs only when **both** the write control is asserted and the clock edge occurs

Creating a Single Datapath from the Parts

- ❑ Assemble the datapath segments, add control lines as needed, and design the control path
- ❑ Fetch, decode and execute each instructions in one clock cycle – single cycle design
 - no datapath resource can be used more than once per instruction, so some must be duplicated (e.g., why we have a separate Instruction Memory and Data Memory)
 - to share datapath elements between two different instruction classes will need multiplexors at the input of the shared elements with control lines to do the selection
- ❑ Cycle time is determined by length of the longest path

Adding the Control

  
- ❑ Selecting the operations to perform (ALU, Register File and Memory read/write)
- ❑ Controlling the flow of data (multiplexor inputs)
- ❑ Information comes from the 32 bits of the instruction



❑ Observations


- op field always in bits 31-26
- addr of two registers to be read are **always** specified by the **rs** and **rt** fields (bits 25-21 and 20-16)
- addr. of register to be written is in one of **two** places – in **rt** (bits 20-16) for lw; in **rd** (bits 15-11) for R-type instructions
- base register for lw and sw always in **rs** (bits 25-21)
- offset for beq, lw, and sw always in bits 15-0

(Almost) Complete Single Cycle Datapath

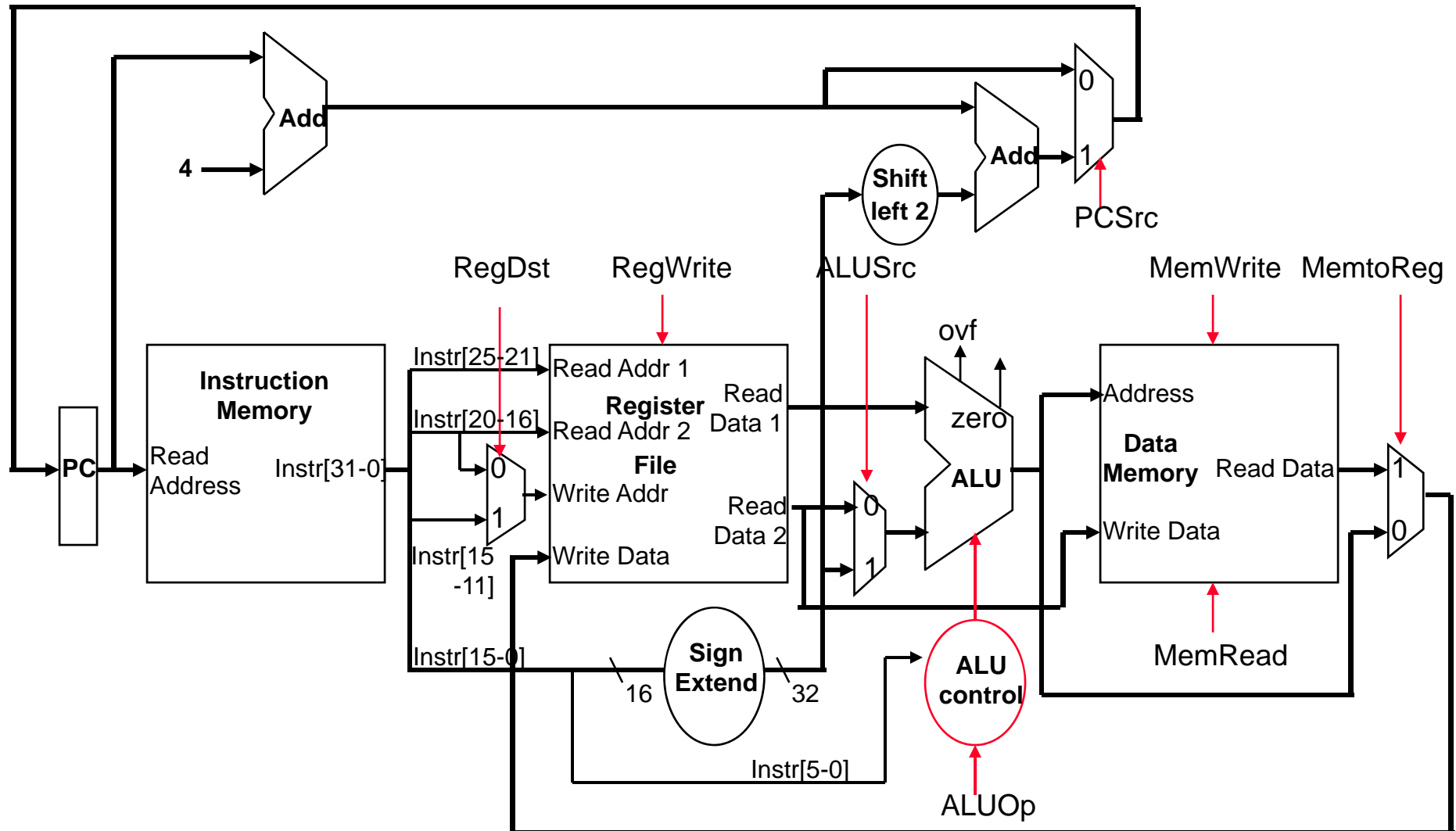


The Main Control Unit

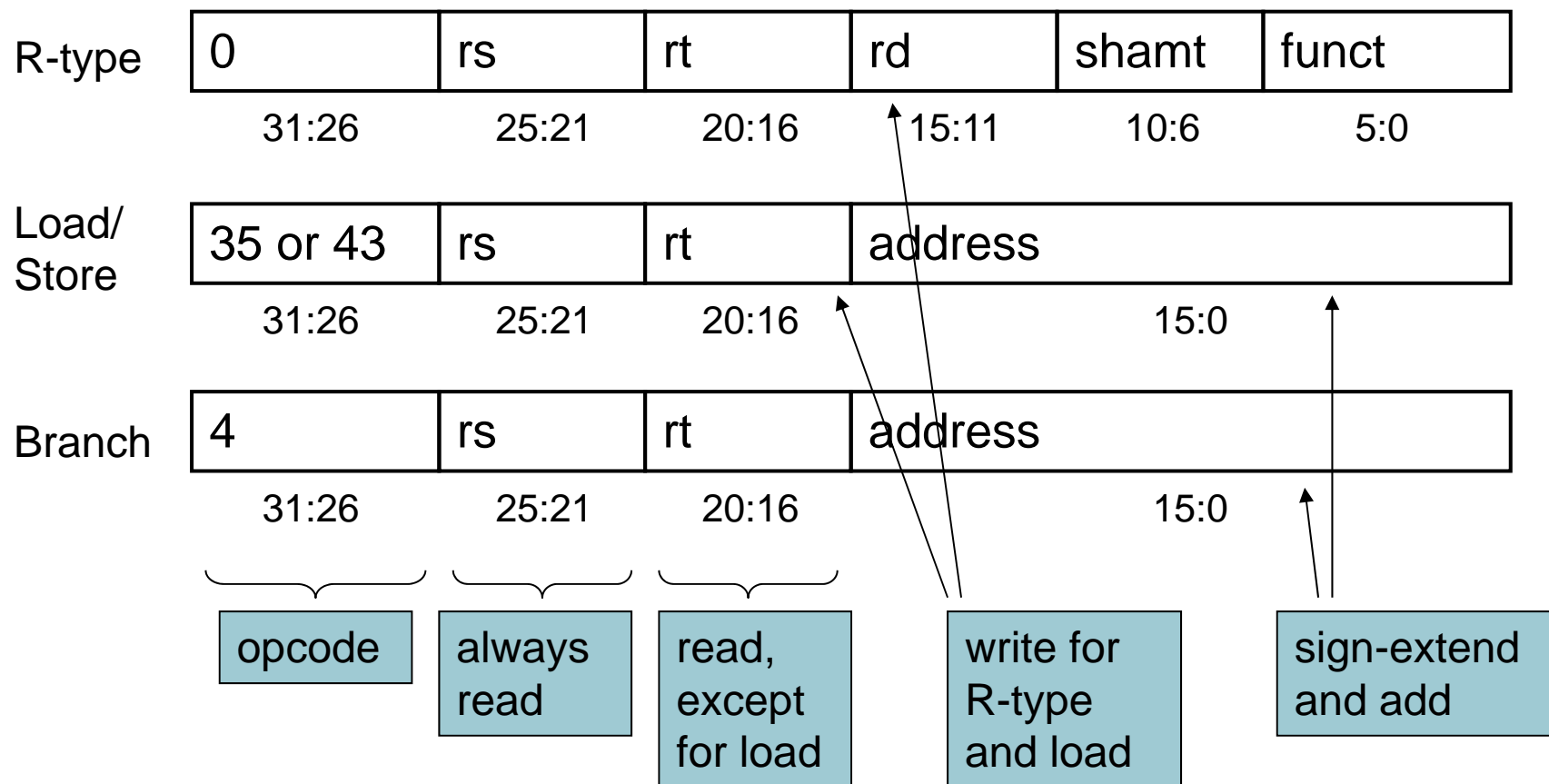
- Control signals derived from instruction



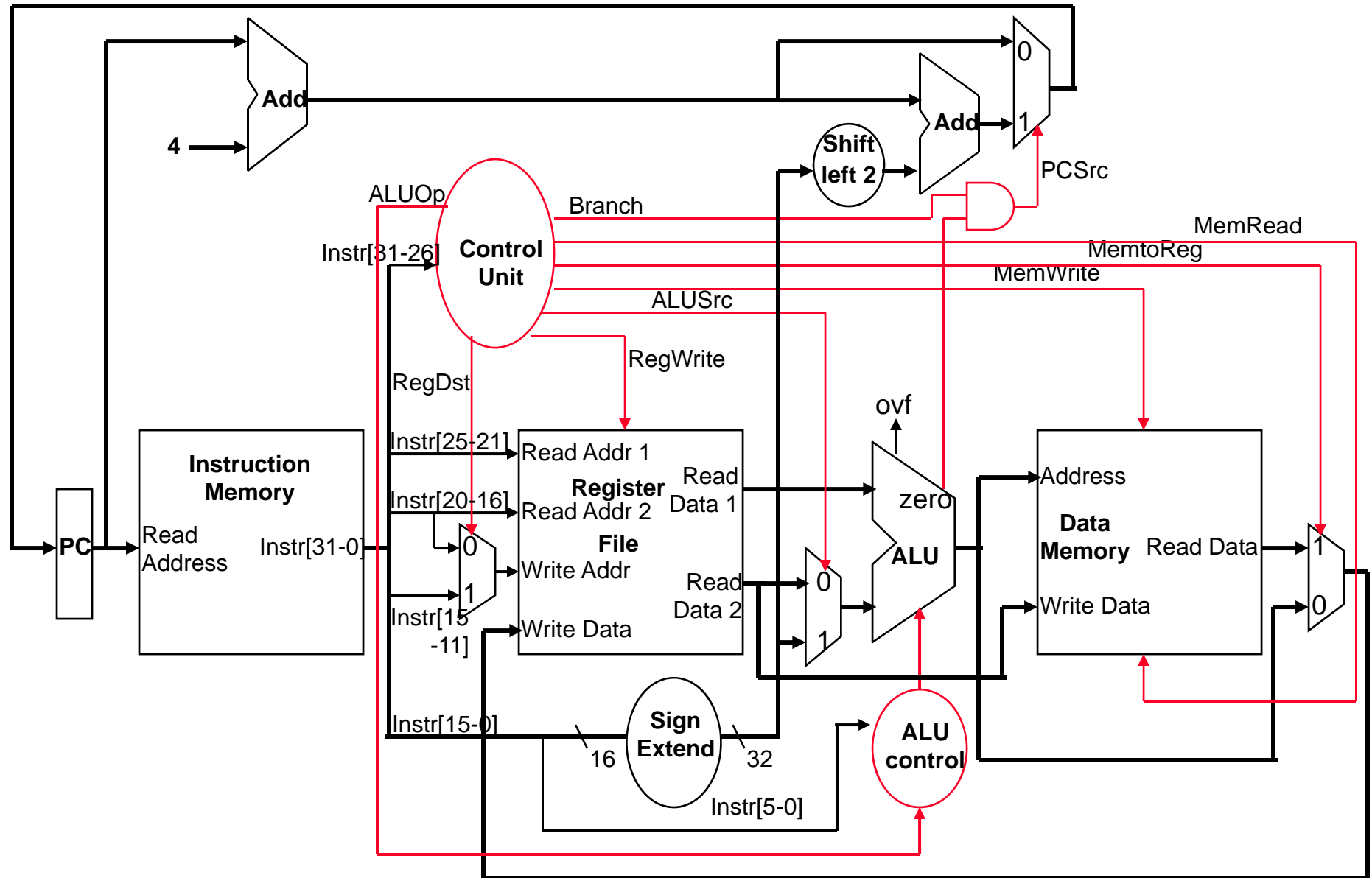
(Almost) Complete Datapath with Control Unit




R-type Instruction Data/Control Flow

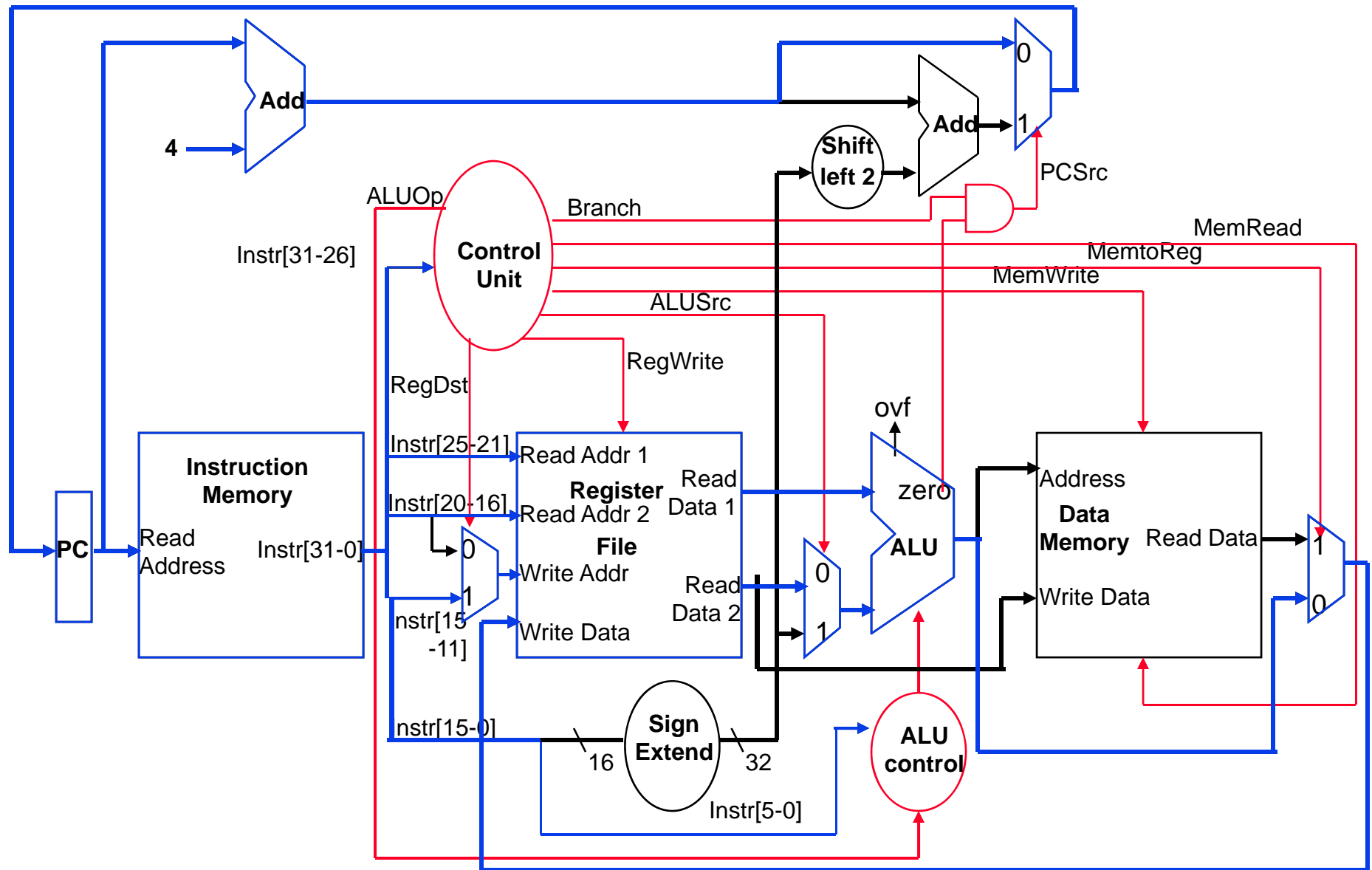


Store Word Instruction Data/Control Flow

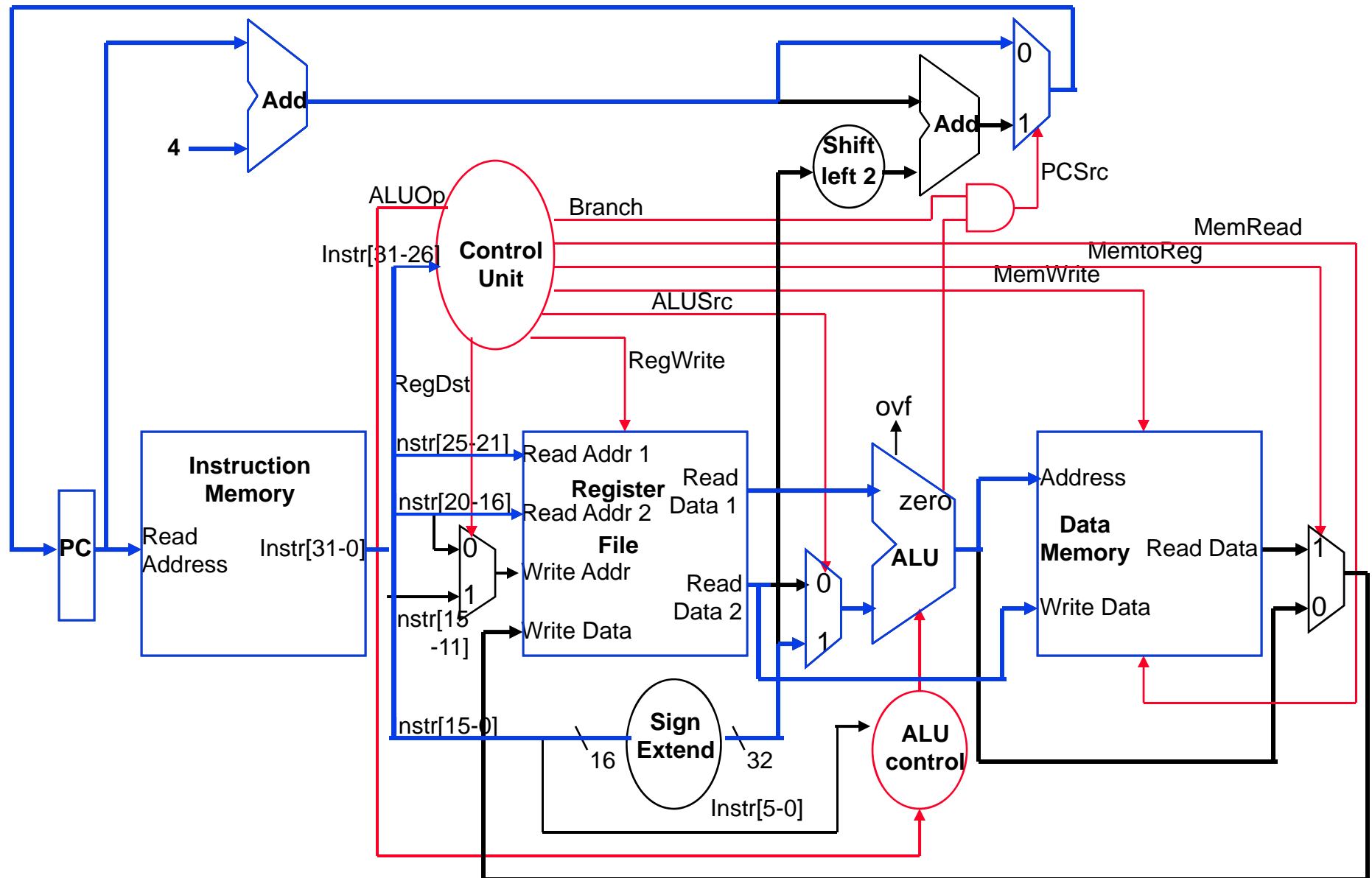

Load Word Instruction Data/Control Flow

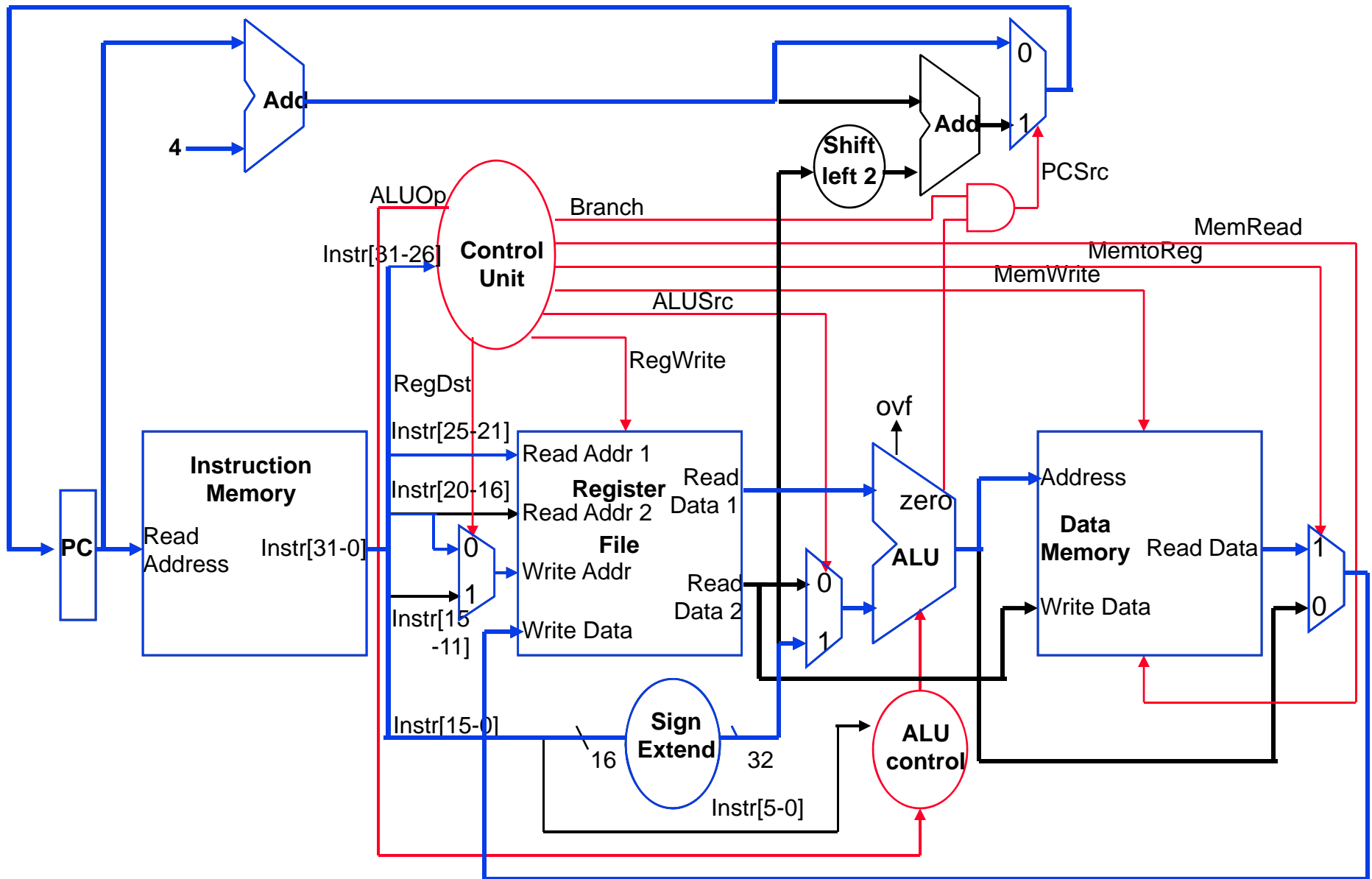

Branch Instruction Data/Control Flow

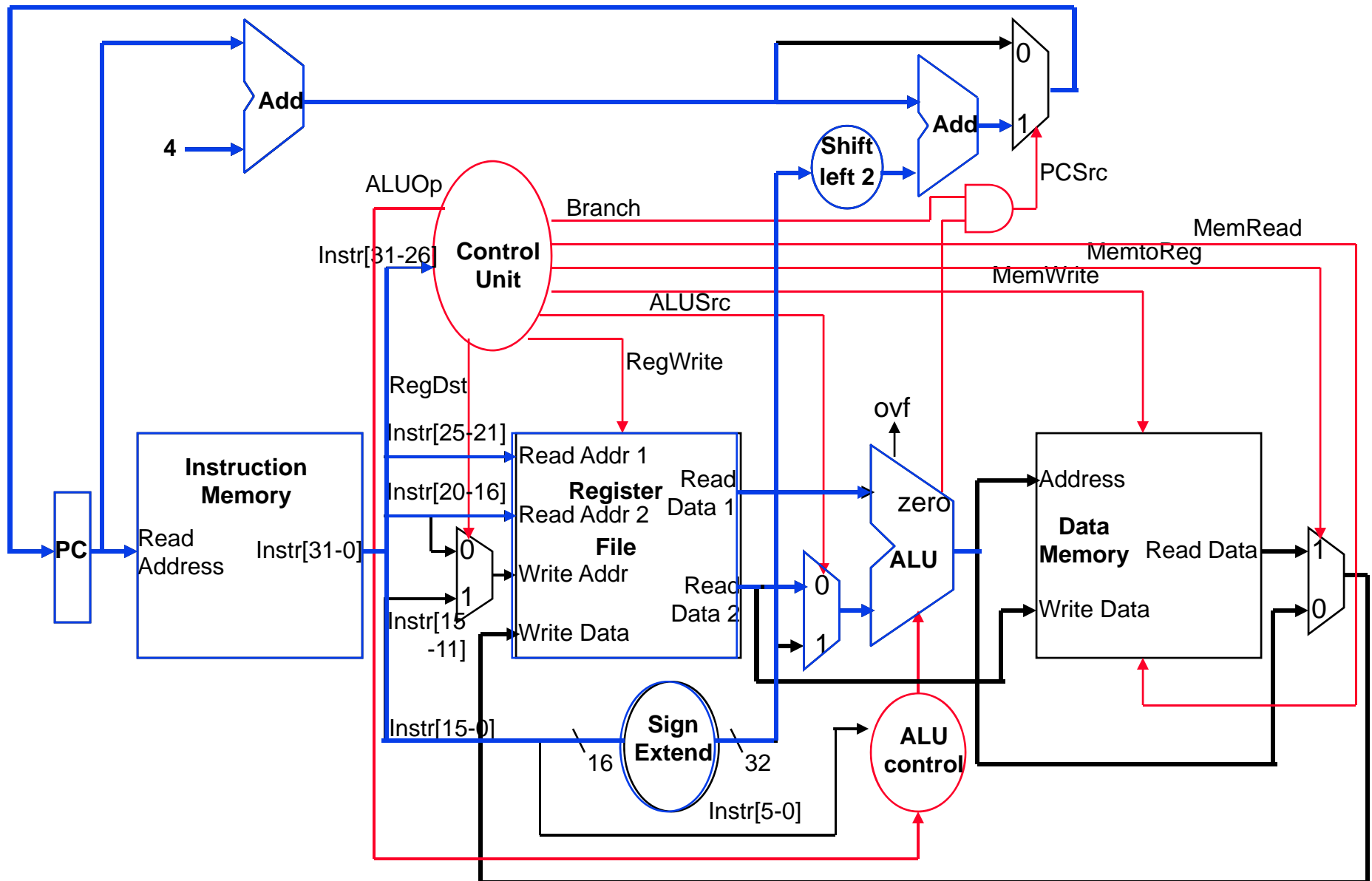

ALU Control

□ ALU used for

- Load/Store: F = add
- Branch: F = subtract
- R-type: F depends on funct field

ALU control	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	set-on-less-than
1100	NOR

ALU Control

- ❑ Assume 2-bit ALUOp derived from opcode
 - Combinational logic derives ALU control


opcode	ALUOp	Operation	funct	ALU function	ALU control
lw	00	load word	XXXXXX	add	0010
sw	00	store word	XXXXXX	add	0010
beq	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
		subtract	100010	subtract	0110
		AND	100100	AND	0000
		OR	100101	OR	0001
		set-on-less-than	101010	set-on-less-than	0111

Main Control Unit

Instr	RegDst	ALUSrc	MemReg	RegWr	MemRd	MemWr	Branch	ALUOp1	ALUOp0
R-type 000000	1	0	0	1	X	0	0	1	0
lw 100011	0	1	1	1	1	0	0	0	0
sw 101011	X	1	X	0	X	1	0	0	0
beq 000100	X	0	X	0	X	0	1	0	1

Control Unit Logic

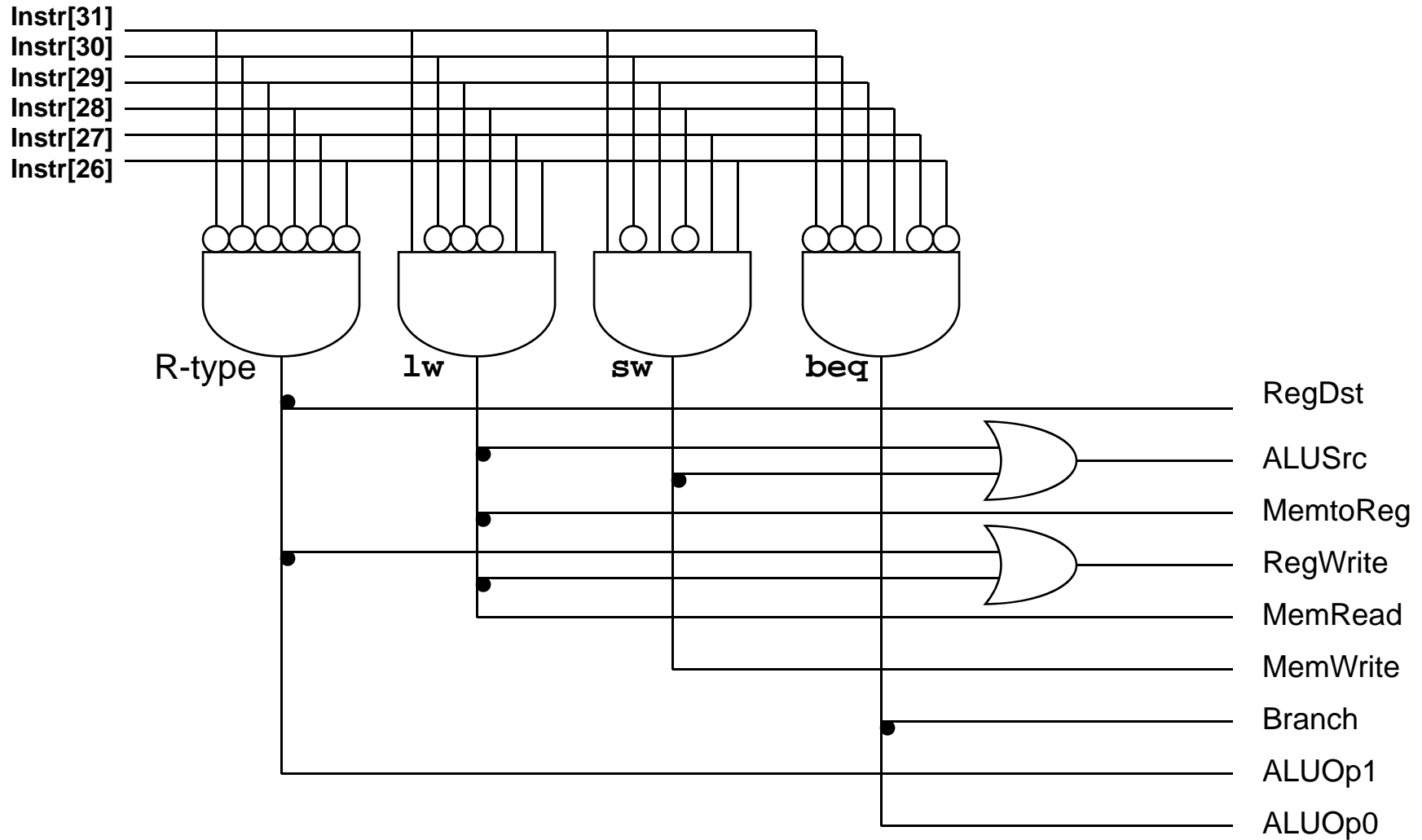- From the truth table can design the Main Control logic



ALU Control Truth Table


F5	F4	F3	F2	F1	F0	ALUOp1	ALUOp0	Op2	Op1	Op0
X	X	X	X	X	X	0	0	0	1	0
X	X	X	X	X	X	0	1	1	1	0
X	X	0	0	0	0	1	0	0	1	0
X	X	0	0	1	0	1	0	1	1	0
X	X	0	1	0	0	1	0	0	0	0
X	X	0	1	0	1	1	0	0	0	1
X	X	1	0	1	0	1	0	1	1	1

❑ Can make use of more don't cares


- since ALUOp does not use the encoding 11
- since F5 and F4 are always 10

❑ Logic comes from the K-maps ...

Adding the Jump Operation

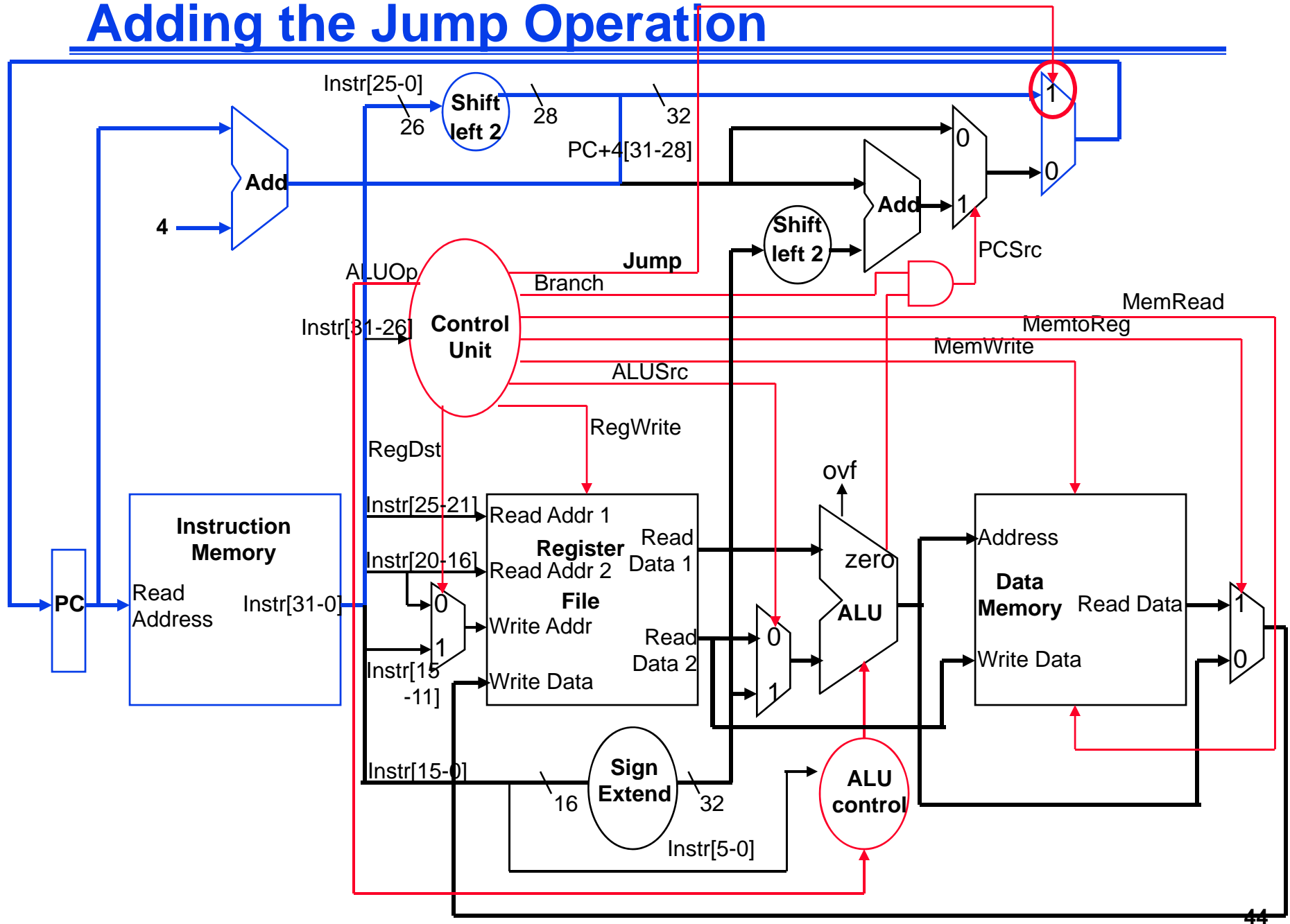

Complete Datapath

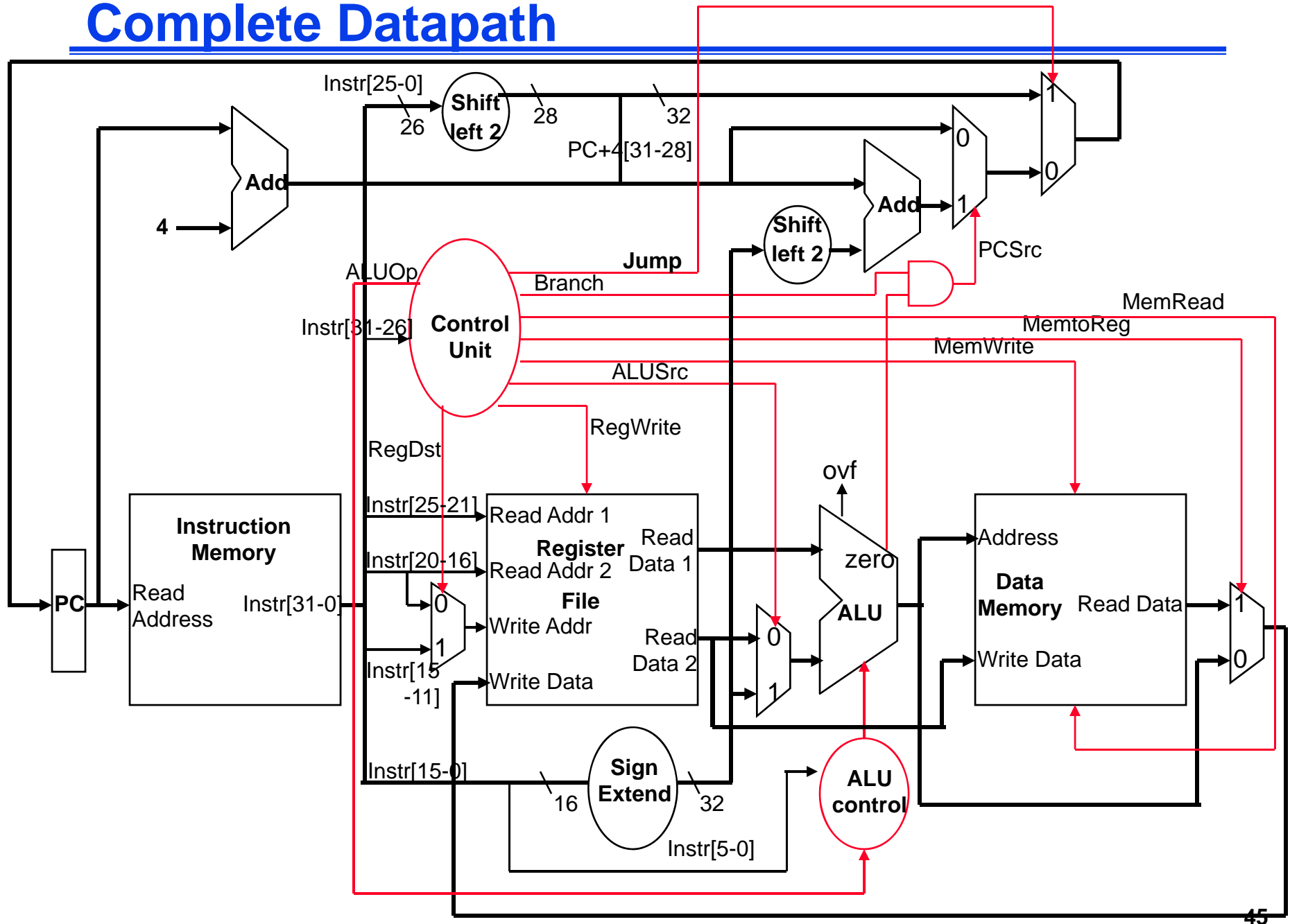

Performance Issues

- Longest delay determines clock period
 - Critical path: load instruction
 - Instruction memory → register file → ALU → data memory → register file
- Not feasible to vary period for different instructions
- Violates design principle
 - Making the common case fast
- We will improve performance by pipelining

Instruction Critical Paths

❑ Calculate cycle time assuming negligible delays (for muxes, control unit, sign extend, PC access, shift left 2, wires) except:

- | Instruction and Data Memory (2ns)
- | ALU and adders (2ns)
- | Register File access (reads or writes) (1ns)

Instr.	I Mem	Reg Rd	ALU Op	D Mem	Reg Wr	Total
R-type	2	1	2		1	6
load	2	1	2	2	1	8
store	2	1	2	2		7
Beq	2	1	2			5
jump	2					2

Question:

- ❑ We wish to add the instruction **addi** to the single-cycle datapath. Add any necessary datapaths and control signals.

Control Signal	Setting	Control Signal	Setting
RegDst		ALUOp1	
Jump		ALUOp0	
Branch		MemWrite	
MemRead		ALUSrc	
MemtoReg		RegWrite	